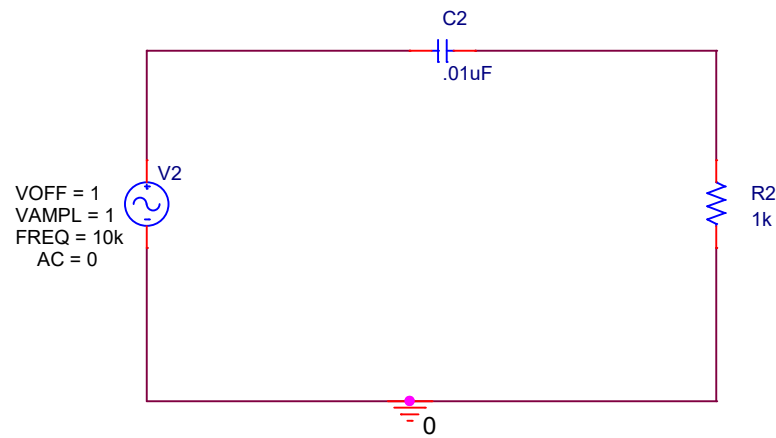



| | A | B | C | D | E | F | G | H | I |
|----|-----------------|--|----------------------|--------------------------|---|------------------------------|--|---------------------------------------|---|
| 1 | Xi Kun Zou | | | | | | | | |
| 2 | Friday | | | | | | | | |
| 3 | | | | | | | | | |
| 4 | PART 1.1 | | | | | | | | |
| 5 | V | C | R | w | | Frequency | | | |
| 6 | =1 | 0.00000001 | 1000 | =E6*2*PI() | | 10000 | | | |
| 7 | | | 2000 | | | | | | |
| 8 | | | 5600 | | | | | | |
| 9 | | | 10000 | | | | | | |
| 10 | | | | | | | | | |
| 11 | 1/wCR | Phase Angle | | | | | | | |
| 12 | =1/(D56*B56*C6) | =ATAN(A12))*(180/PI()) | | | | | | | |
| 13 | =1/(D56*B56*C7) | =ATAN(A13))*(180/PI()) | | | | | | | |
| 14 | =1/(D56*B56*C8) | =ATAN(A14))*(180/PI()) | | | | | | | |
| 15 | =1/(D56*B56*C9) | =ATAN(A15))*(180/PI()) | | | | | | | |
| 16 | | | | | | | | | |
| 17 | 1.2 | | | | | | | | |
| 18 | Frequency | w | wCR | Vout | | | | | |
| 19 | 1000 | =A19*2*PI() | =B19*B56*1000 | =(C19/(SQRT((C19)^2+1))) | | | | | |
| 20 | 10000 | =A20*2*PI() | =B20*B56*1000 | =(C20/(SQRT((C20)^2+1))) | | | | | |
| 21 | 100000 | =A21*2*PI() | =B21*B56*1000 | =(C21/(SQRT((C21)^2+1))) | | | | | |
| 22 | | | | | | | | | |
| 23 | 1.3 | | | | | | | | |
| 24 | R | Frequency | C | W | N | D | Phase Angle N | Phase Angle (D) | Phase Difference |
| 25 | 1000 | 10000 | 0.00000001 | =B25*2*PI() | 1 | =SQRT((D525*CS25*A25)^2+1) | =0 | =(ATAN((D525*CS25*A25/1))*(180/PI())) | =G25-H25 |
| 26 | 2000 | | | | 1 | =SQRT((D525*CS25*A26)^2+1) | =0 | =(ATAN((D525*CS25*A26/1))*(180/PI())) | =G26-H26 |
| 27 | 5600 | | | | 1 | =SQRT((D525*CS25*A27)^2+1) | =0 | =(ATAN((D525*CS25*A27/1))*(180/PI())) | =G27-H27 |
| 28 | 10000 | | | | 1 | =SQRT((D525*CS25*A28)^2+1) | =0 | =(ATAN((D525*CS25*A28/1))*(180/PI())) | =G28-H28 |
| 29 | | | | | | | | | |
| 30 | 1.4 | | | | | | | | |
| 31 | R | Frequency | C | w | N | D | Vout | | |
| 32 | 1000 | 1000 | 0.00000001 | =B32*2*PI() | 1 | =SQRT((D32*CS32*AS32)^2+1) | =E32/F32 | | |
| 33 | | 10000 | | =B33*2*PI() | 1 | =SQRT((D33*CS32*AS32)^2+1) | =E33/F33 | | |
| 34 | | 100000 | | =B34*2*PI() | 1 | =SQRT((D34*CS32*AS32)^2+1) | =E34/F34 | | |
| 35 | | | | | | | | | |
| 36 | PART 2.1 | | | | | | | | |
| 37 | R | Frequency | L | w | N | D | Vout | | |
| 38 | 1000 | 1000 | 0.047 | =B38*2*PI() | =D38*CS38 | =SQRT((AS38^2)+(D38*CS38)^2) | =E38/F38 | | |
| 39 | | 10000 | | =B39*2*PI() | =D39*CS38 | =SQRT((AS38^2)+(D39*CS38)^2) | =E39/F39 | | |
| 40 | | 100000 | | =B40*2*PI() | =D40*CS38 | =SQRT((AS38^2)+(D40*CS38)^2) | =E40/F40 | | |
| 41 | | | | | | | | | |
| 42 | 2.2 | | | | | | | | |
| 43 | R | Frequency | L | w | N | D | Vout | | |
| 44 | 1000 | 1000 | 0.047 | =B44*2*PI() | =AS44 | =SQRT((AS44^2)+(D44*CS44)^2) | =E44/F44 | | |
| 45 | | 10000 | | =B45*2*PI() | =AS44 | =SQRT((AS44^2)+(D45*CS44)^2) | =E45/F45 | | |
| 46 | | 100000 | | =B46*2*PI() | =AS44 | =SQRT((AS44^2)+(D46*CS44)^2) | =E46/F46 | | |
| 47 | | | | | | | | | |
| 48 | PART 3.2 | | | | | | | | |
| 49 | Frequency | R | L | C | w | N | D | Phase Angle(N) | Phase Angle(D) |
| 50 | 5000 | 270 | 0.047 | 0.00000001 | =AS50*2*PI() | =BS50 | =SQRT((BS50^2)+((ES50*CS50)-(1/(ES50*DS50))))^2) | =ATAN(0/270) | =(ATAN(((ES50*CS50)-(1/(ES50*DS50)))/BS50))*(180/PI())) |
| 51 | | | | | | | | | |
| 52 | 3.3 | | | | | | | | |
| 53 | Frequency | R | L | C | w | N | D | Phase Angle(N) | Phase Angle(D) |
| 54 | 5000 | 270 | 0.047 | =0.047*10^-6 | =AS54*2*PI() | =BS54 | =SQRT((BS54^2)+((ES54*CS54)-(1/(ES54*DS54))))^2) | =ATAN(0/BS54) | =(ATAN(((ES54*CS54)-(1/(ES54*DS54)))/BS54))*(180/PI())) |
| 55 | | | | | | | | | |
| 56 | PART 4 | | | | | | | | |
| 57 | Frequency | R | c | w | N | D | Phase Angle(N) | Phase Angle(D) | |
| 58 | 10000 | 910 | =1*10^-8 | =AS58*2*PI() | =1 | =SQRT((ES58)^2+1) | =ATAN(0/1) | =(ATAN(D558*CS58/BS58/1))*(180/PI())) | |
| 59 | | | | | | | | | |
| 60 | PART 5.1 | | | | | | | | |
| 61 | Vo/Vi | phase | | | | | | | |
| 62 | 3 | 0 | | | | | | | |
| 63 | 5.2 | | | | | | | | |
| 64 | C | R | | 1/wC | | | | | |
| 65 | 0.00000001 | 100000 | | =1/(10000*2*PI()*A65) | | | | | |
| 66 | | | | | | | | | |
| 67 | R | N | D | Vout/Vin | Phase Angle(N) | Phase Angle(D) | Phase Difference | | |
| 68 | 1000 | =SQRT((BS65*CS65^2)^2+(BS65^2*CS65^2)^2) | =(BS65^2+CS65^2)*A68 | =1+B68/C68 | =DEGREES(ATAN2(B=DEGREES(ATAN2(C68,0))) | | =E68-F68 | | |
| 69 | 2000 | =SQRT((BS65*CS65^2)^2+(BS65^2*CS65^2)^2) | =(BS65^2+CS65^2)*A69 | =1+B69/C69 | =DEGREES(ATAN2(B=DEGREES(ATAN2(C69,0))) | | =E69-F69 | | |
| 70 | 5600 | =SQRT((BS65*CS65^2)^2+(BS65^2*CS65^2)^2) | =(BS65^2+CS65^2)*A70 | =1+B70/C70 | =DEGREES(ATAN2(B=DEGREES(ATAN2(C70,0))) | | =E70-F70 | | |
| 71 | 10000 | =SQRT((BS65*CS65^2)^2+(BS65^2*CS65^2)^2) | =(BS65^2+CS65^2)*A71 | =1+B71/C71 | =DEGREES(ATAN2(B=DEGREES(ATAN2(C71,0))) | | =E71-F71 | | |

| | A | B | C | D | E | F | G | H | I |
|----|------------|------------------|------------|------------|----------------|----------------|------------------|-----------------|------------------|
| 1 | Xi Kun Zou | | | | | | | | |
| 2 | Friday | | | | | | | | |
| 3 | | | | | | | | | |
| 4 | PART 1.1 | | | | | | | | |
| 5 | V | C | R | w | Frequency | | | | |
| 6 | 1 | 1.00E-08 | 1000 | 62831.8531 | 10000 | | | | |
| 7 | | | 2000 | | | | | | |
| 8 | | | 5600 | | | | | | |
| 9 | | | 10000 | | | | | | |
| 10 | | | | | | | | | |
| 11 | 1/wCR | Phase Difference | | | | | | | |
| 12 | 1.59E+00 | 57.85809236 | | | | | | | |
| 13 | 7.96E-01 | 38.51188725 | | | | | | | |
| 14 | 2.84E-01 | 15.86542838 | | | | | | | |
| 15 | 1.59E-01 | 9.043061079 | | | | | | | |
| 16 | | | | | | | | | |
| 17 | 1.2 | | | | | | | | |
| 18 | Frequency | w | wCR | Vout | | | | | |
| 19 | 1000 | 6283.185307 | 6.28E-02 | 0.06270819 | | | | | |
| 20 | 10000 | 62831.85307 | 6.28E-01 | 0.53201804 | | | | | |
| 21 | 100000 | 628318.5307 | 6.28E+00 | 0.98757049 | | | | | |
| 22 | | | | | | | | | |
| 23 | 1.3 | | | | | | | | |
| 24 | R | Frequency | C | W | N | D | Phase Angle N | Phase Angle (D) | Phase Difference |
| 25 | 1000 | 10000 | 1.00E-08 | 6.28E+04 | 1 | 1.181009812 | 0 | 32.14190764 | -32.14190764 |
| 26 | 2000 | | | | 1 | 1.605969086 | 0 | 51.48811275 | -51.48811275 |
| 27 | 5600 | | | | 1 | 3.657927249 | 0 | 74.13457162 | -74.13457162 |
| 28 | 10000 | | | | 1 | 6.362265132 | 0 | 80.95693892 | -80.95693892 |
| 29 | | | | | | | | | |
| 30 | 1.4 | | | | | | | | |
| 31 | R | Frequency | C | w | N | D | Vout | | |
| 32 | 1000 | 1000 | 1.00E-08 | 6283.18531 | 1 | 1.001971977 | 0.998031905 | | |
| 33 | | 10000 | | 62831.8531 | 1 | 1.181009812 | 0.846733016 | | |
| 34 | | 100000 | | 628318.531 | 1 | 6.362265132 | 0.157176725 | | |
| 35 | | | | | | | | | |
| 36 | PART 2.1 | | | | | | | | |
| 37 | R | Frequency | L | w | N | D | Vout | | |
| 38 | 1000 | 1000 | 0.047 | 6283.18531 | 295.3097094 | 1042.692584 | 0.283218385 | | |
| 39 | | 10000 | | 62831.8531 | 2953.097094 | 3117.816936 | 0.947168212 | | |
| 40 | | 100000 | | 628318.531 | 29530.97094 | 29547.89747 | 0.99942715 | | |
| 41 | | | | | | | | | |
| 42 | 2.2 | | | | | | | | |
| 43 | R | Frequency | L | w | N | D | Vout | | |
| 44 | 1000 | 1000 | 0.047 | 6283.18531 | 1000 | 1042.692584 | 0.959055445 | | |
| 45 | | 10000 | | 62831.8531 | 1000 | 3117.816936 | 0.32073724 | | |
| 46 | | 100000 | | 628318.531 | 1000 | 29547.89747 | 0.033843356 | | |
| 47 | | | | | | | | | |
| 48 | PART 3.2 | | | | | | | | |
| 49 | Frequency | R | L | C | w | N | D | Phase Angle(N) | Phase Angle(D) |
| 50 | 5000 | 270 | 0.047 | 1.00E-08 | 31415.92654 | 270 | 1727.777178 | 0 | -81.00953174 |
| 51 | | | | | | | | | |
| 52 | 3.3 | | | | | | | | |
| 53 | Frequency | R | L | C | w | N | D | Phase Angle(N) | Phase Angle(D) |
| 54 | 5000 | 270 | 0.047 | 4.7E-08 | 31415.92654 | 270 | 843.6646558 | 0 | 71.33511745 |
| 55 | | | | | | | | | |
| 56 | PART 4 | | | | | | | | |
| 57 | Frequency | R | c | w | N | D | Phase Angle(N) | Phase Angle(D) | |
| 58 | 10000 | 910 | 0.00000001 | 62831.8531 | 1 | 1.414213562 | 0 | 29.75962026 | |
| 59 | | | | | | | | | |
| 60 | PART 5.1 | | | | | | | | |
| 61 | Vo/Vi | phase | | | | | | | |
| 62 | 3 | 0 | | | | | | | |
| 63 | 5.2 | | | | | | | | |
| 64 | C | R | 1/wC | | | | | | |
| 65 | 1E-08 | 100000 | 1591.54943 | | | | | | |
| 66 | | | | | | | | | |
| 67 | R | N | D | Vout/Vin | Phase Angle(N) | Phase Angle(D) | Phase Difference | | |
| 68 | 1000 | 1.59175E+13 | 1.0003E+13 | 2.5913479 | 57.20254411 | 0 | 57.20254411 | | |
| 69 | 2000 | 1.59175E+13 | 2.0005E+13 | 1.79567395 | 38.15408643 | 0 | 38.15408643 | | |
| 70 | 5600 | 1.59175E+13 | 5.6014E+13 | 1.28416927 | 15.79377756 | 0 | 15.79377756 | | |


| | A | B | C | D | E | F | G | H | I |
|----|-------|-------------|------------|------------|-------------|---|-------------|---|---|
| 71 | 10000 | 1.59175E+13 | 1.0003E+14 | 1.15913479 | 9.018347633 | 0 | 9.018347633 | | |





| | | |
|---------------------|-----------------------------|------------------|
| | | |
| Title Xi Kun Zou | | |
| Size A | Document Number Prelab 2 | Rev <RevCode> |
| Date: | Friday, March 03, 2017 | Sheet 1 of 1 |

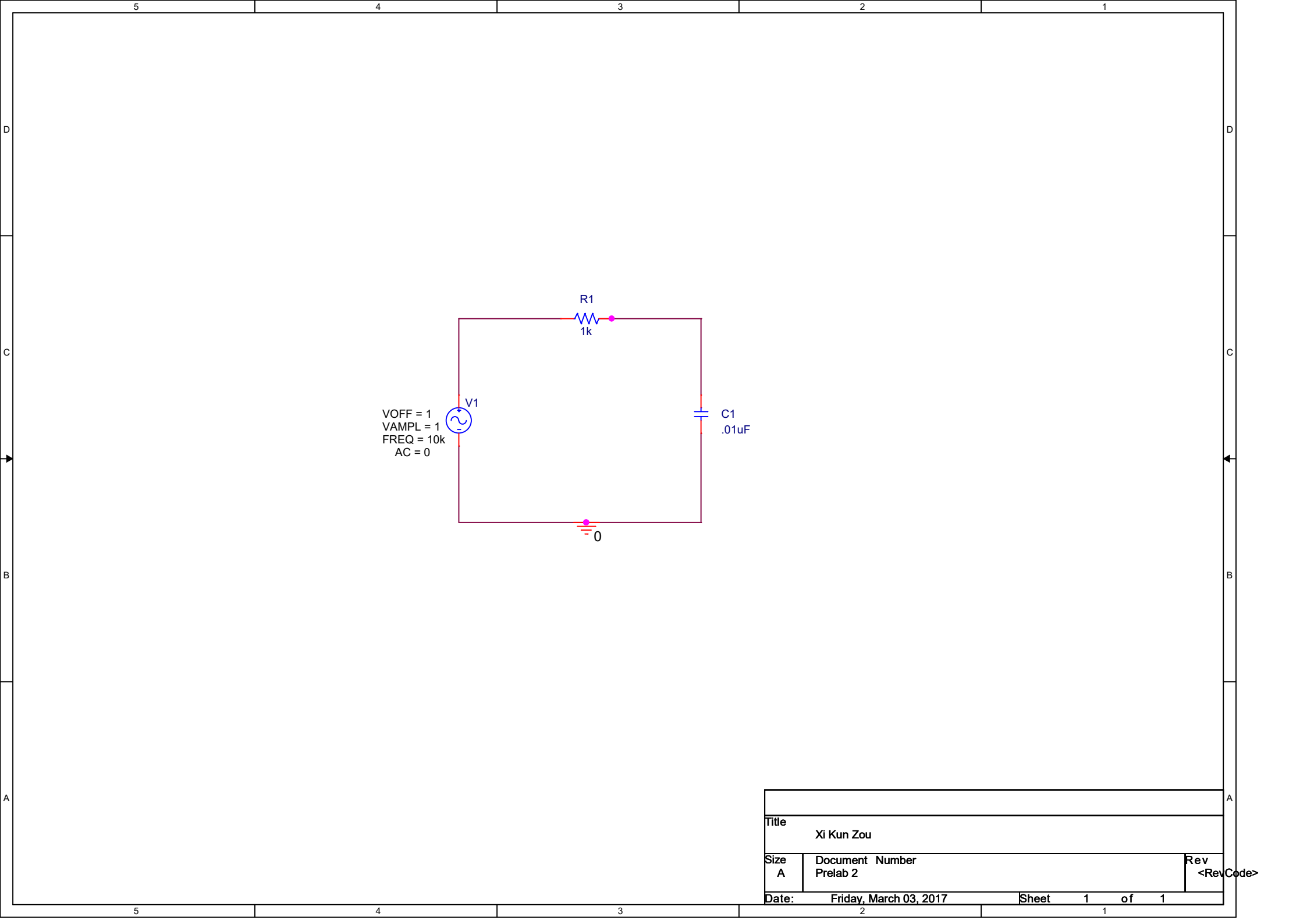


| | | | |
|------------|------------------------|--------|--------------|
| | | | |
| Title | | | |
| Xi Kun Zou | | | |
| Size | Document | Number | Rev |
| A | Prelab 2 | | <RevCode> |
| Date: | Friday, March 03, 2017 | | Sheet 1 of 1 |

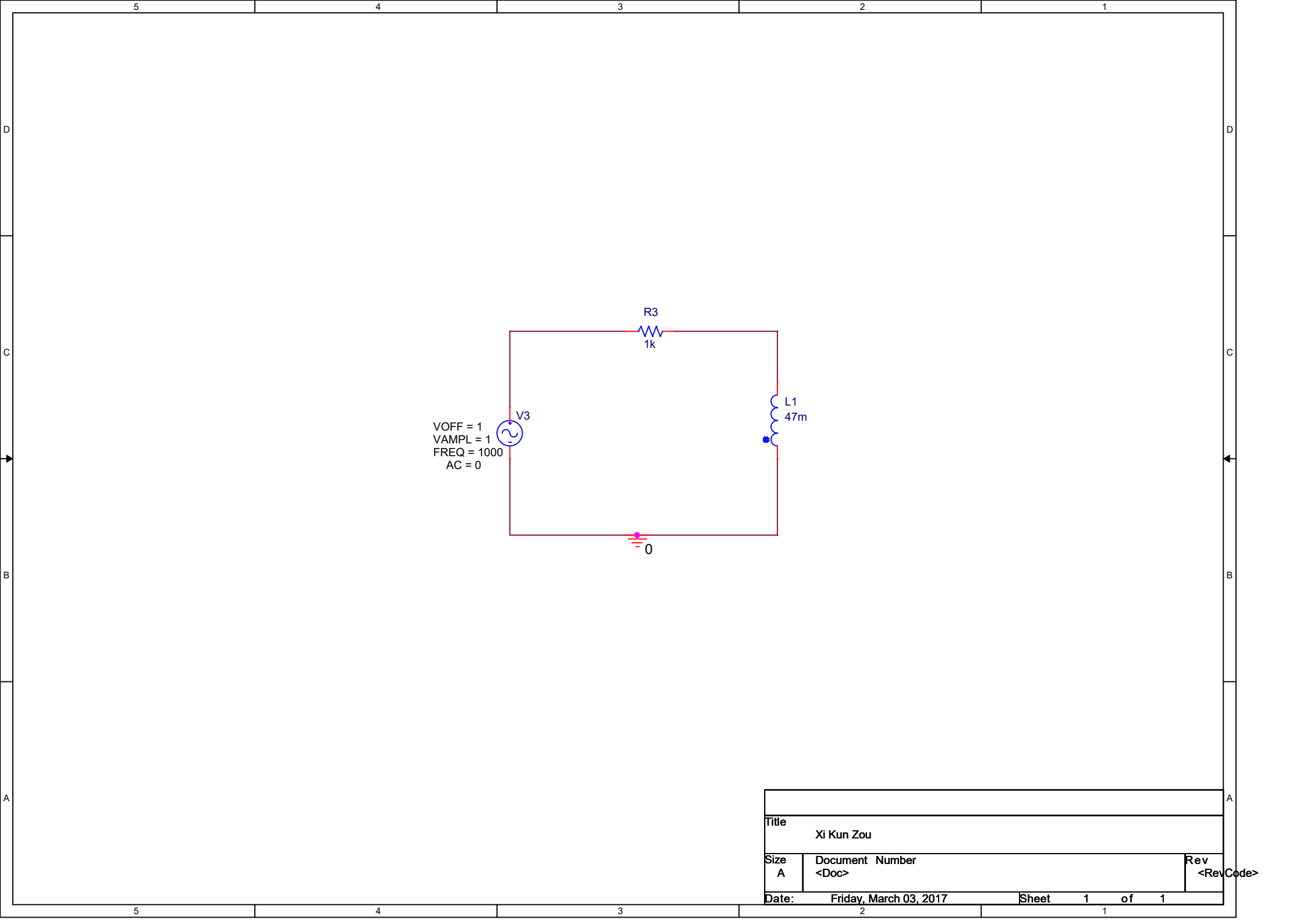


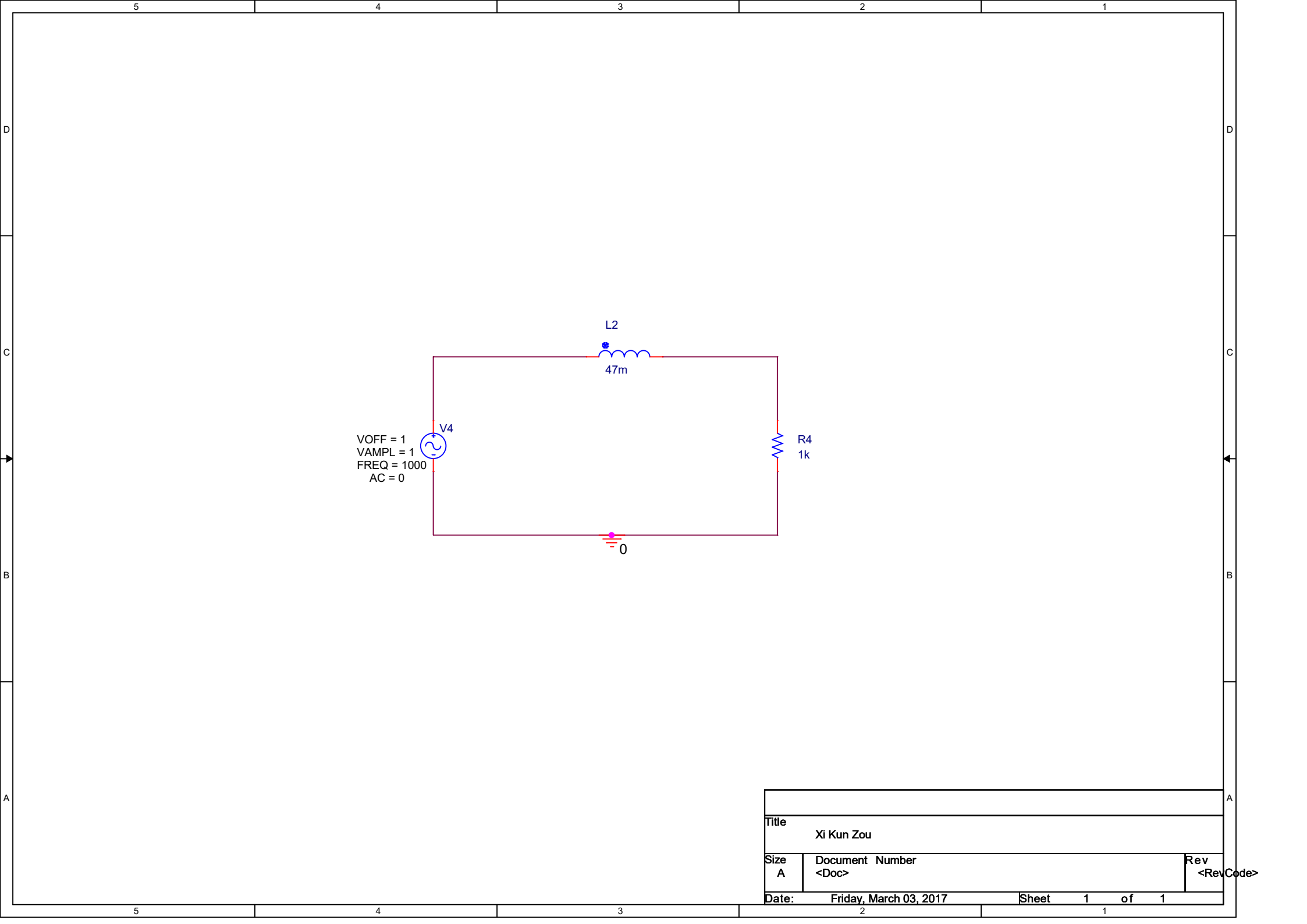

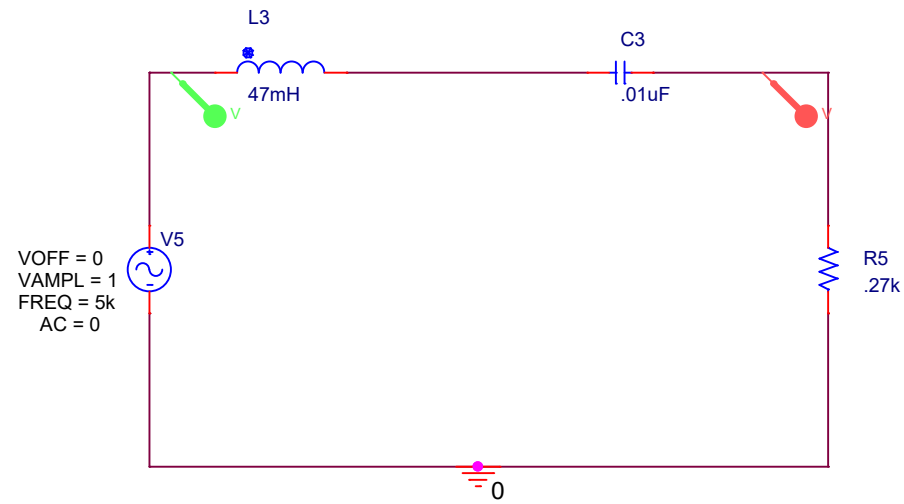


| | | | |
|------------|------------------------|--------|--------------|
| | | | |
| Title | | | |
| Xi Kun Zou | | | |
| Size | Document | Number | Rev |
| A | <Doc> | | <RevCode> |
| Date: | Friday, March 03, 2017 | | Sheet 1 of 1 |

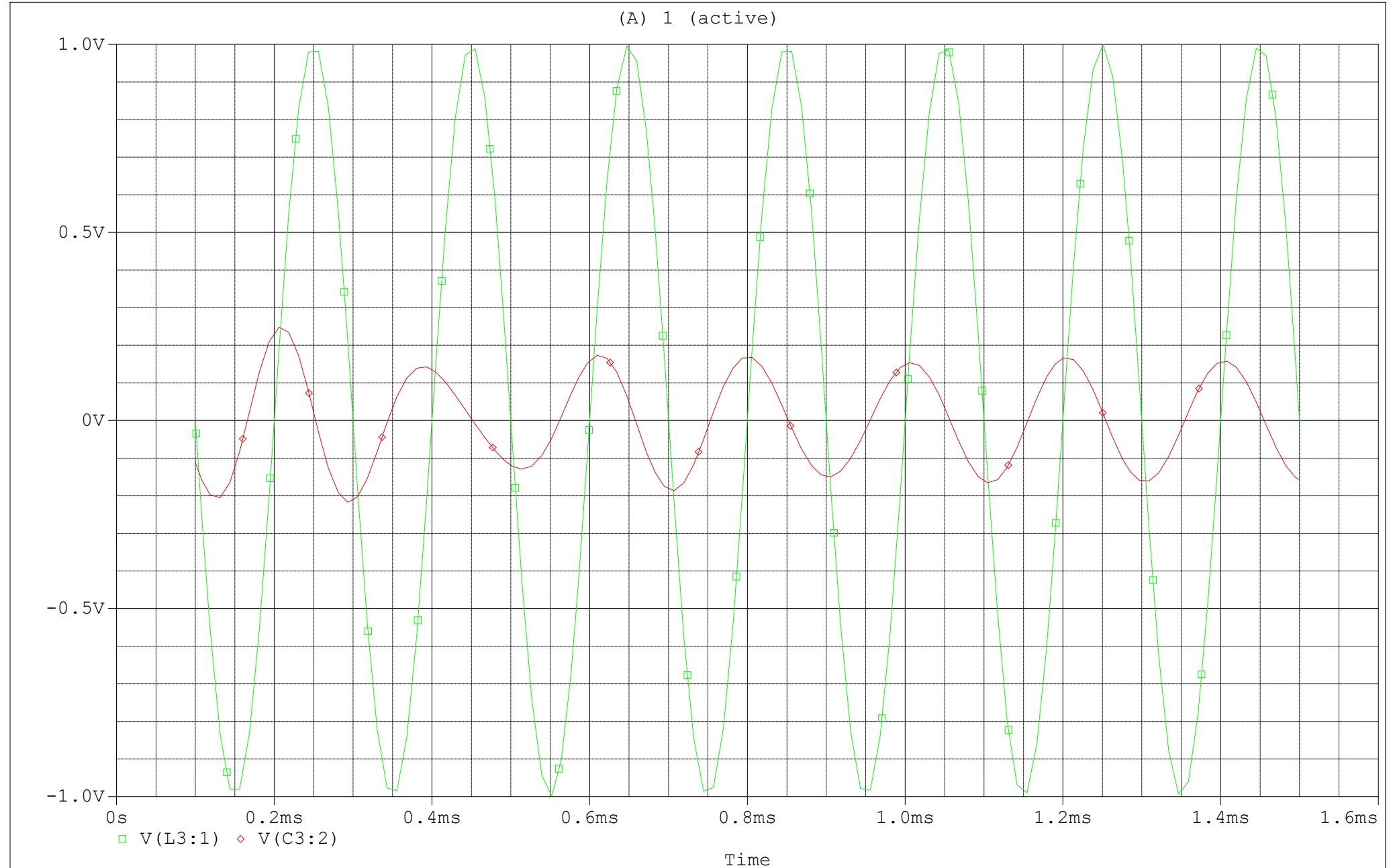


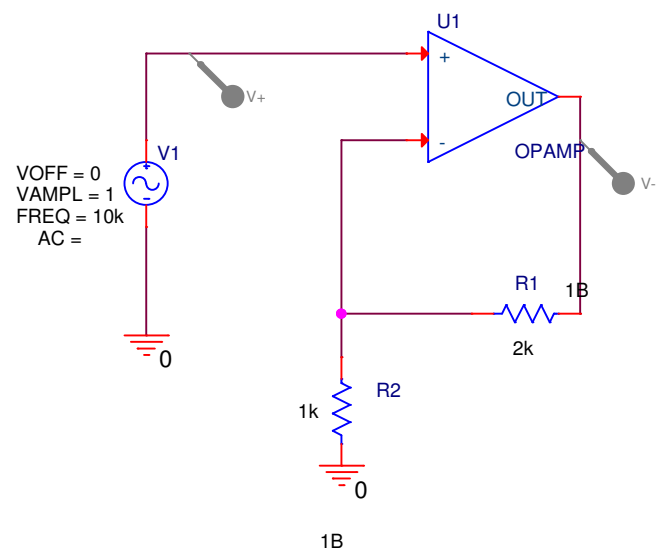


| | | |
|------------|------------------------|--------------|
| Title | | |
| Xi Kun Zou | | |
| Size | Document Number | Rev |
| A | <Doc> | <RevCo |
| Date: | Friday, March 03, 2017 | Sheet 1 of 1 |

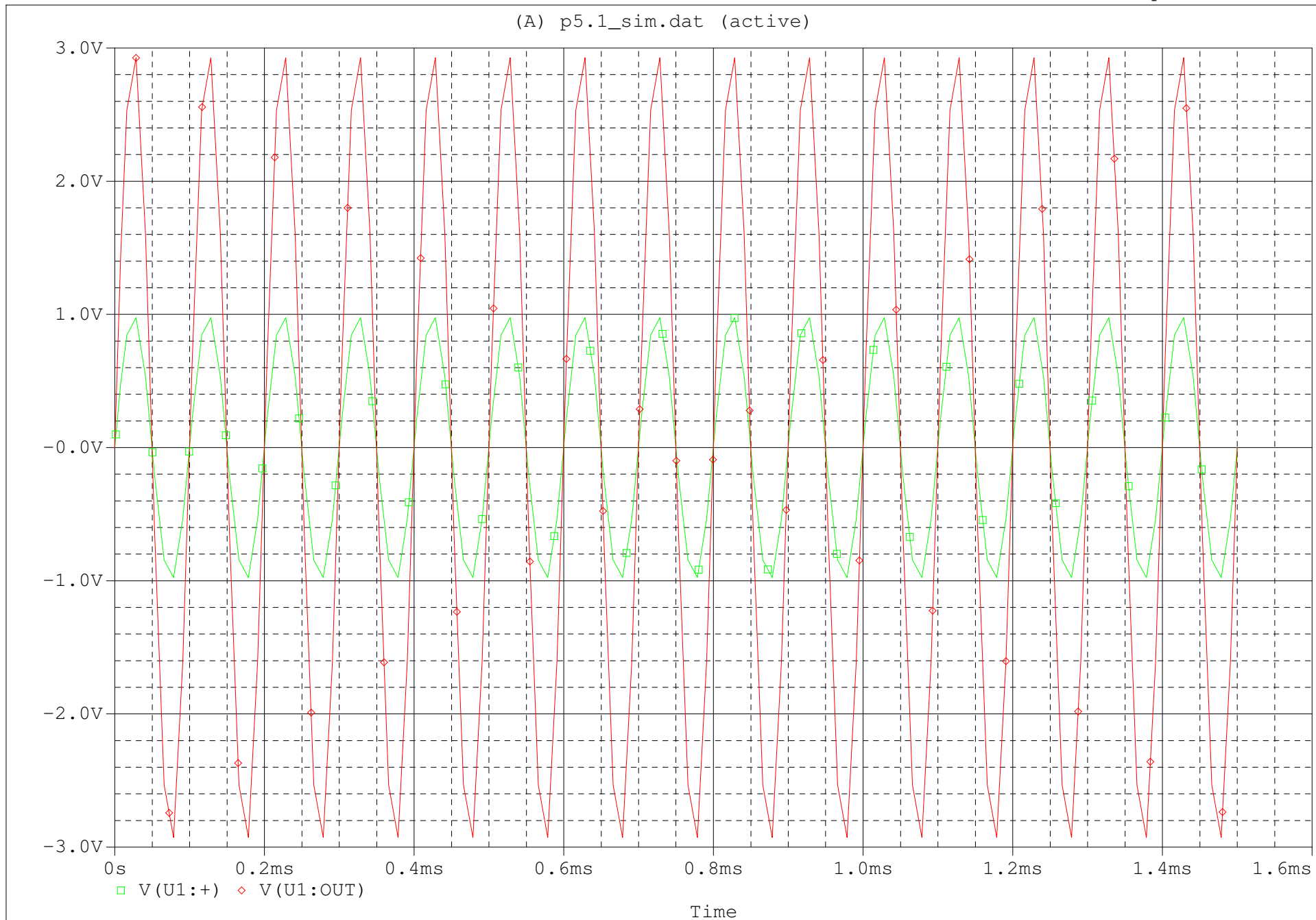** Profile: "SCHEMATIC1-p5.1_sim" [C:\PExcercise\Lab2-PSpiceFiles\SCHEMATIC1\p5.1_sim.sim]
Date/Time run: 03/03/17 12:46:42 Temperature: 27.0



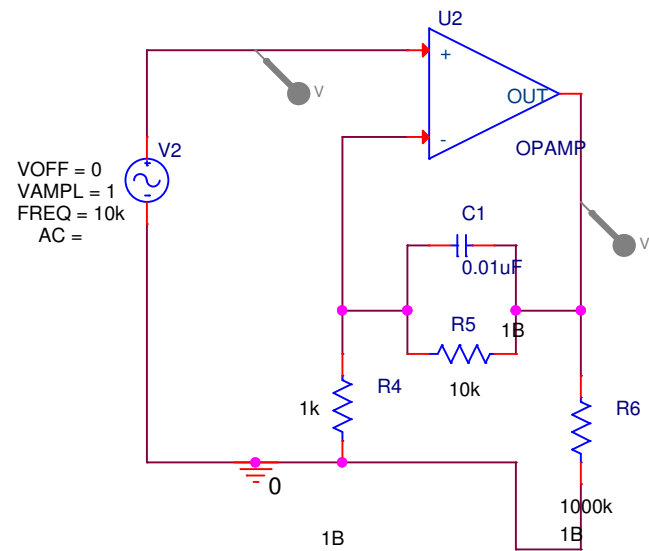

| | | |
|------------|------------------------|--------------|
| Title | | |
| Xi Kun Zou | | |
| Size | Document Number | Rev |
| A | <Doc> | <RevCo> |
| Date: | Friday, March 03, 2017 | Sheet 1 of 1 |

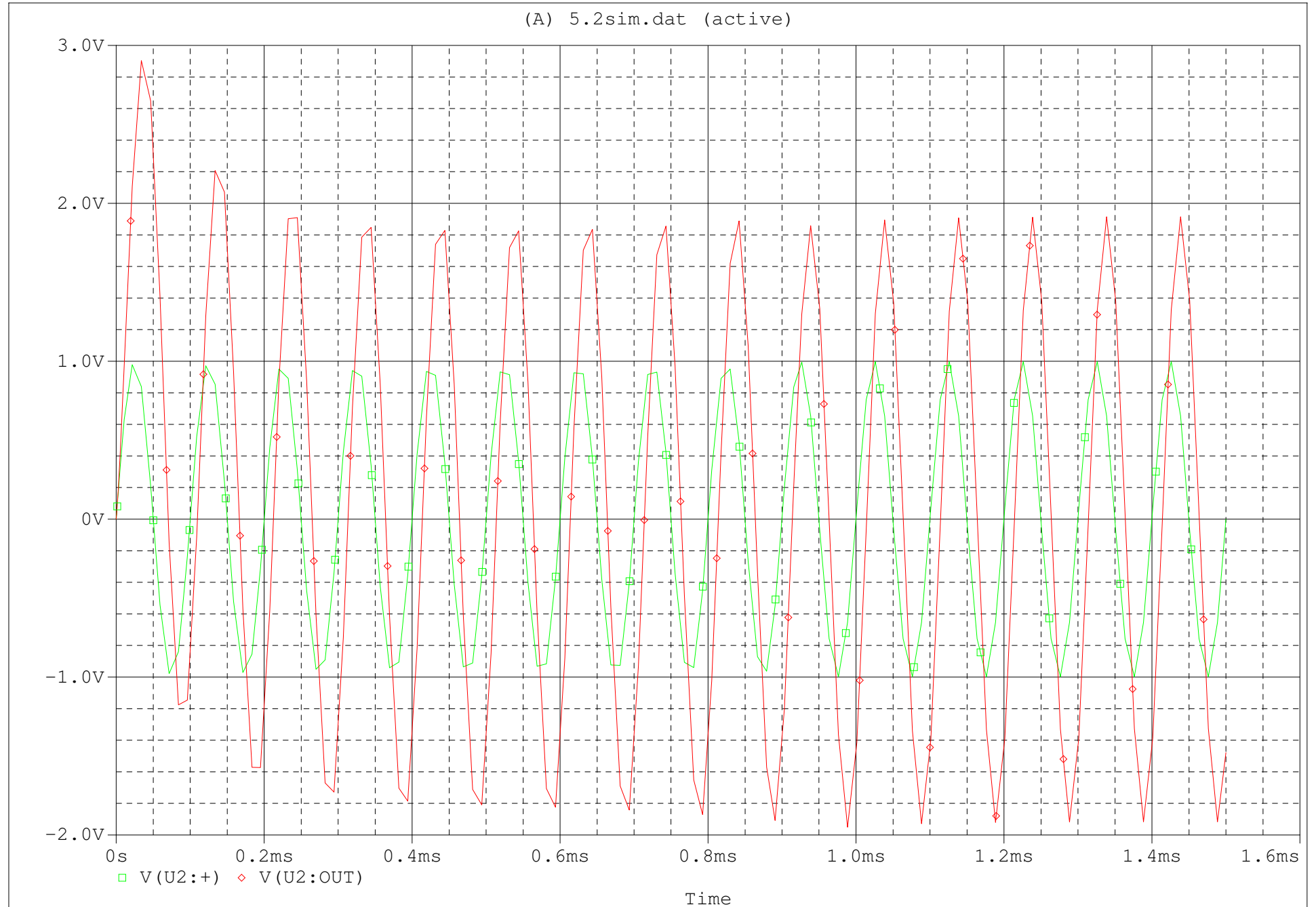

17
20

Lab 2: Gain and Phase Measurements of RC, RL, and RLC Networks

Objectives

In this lab exercise you will analyze and measure the phase and amplitude relationships of input voltages and responses in circuits comprised of resistors, capacitors, and inductors. An op-amp with a capacitor in the feedback loop will also be analyzed and measured. Prior to performing the lab, you will analyze each circuit by hand and check your results using PSpice.

The purpose of the pre-lab work is to make sure you understand how each circuit works and what results to expect when you make measurements in the lab. This should allow you to spend nearly all of your time in the lab building circuits and making measurements. If you know what results to expect, you will know when you have done each experiment correctly. If your hand calculations and PSpice results agree, you will know that your pre-lab work is correct.

Pre-Lab Instructions (10pts)

Calculations and comparisons

1. Using circuit analysis techniques such as nodal analysis and/or voltage dividers with phasors, calculate the theoretical gains and phase relationships asked for in each part of this lab (see the Appendix A for an example). **All calculations should be shown on a separate sheet to be handed in;** that is, your results should **not** be recorded in the spaces designated throughout this assignment until you are in lab (or just before lab) and comparing your prelab results with those of your lab partner. You must use Excel to speed up these hand calculations. In other words, program each formula once, then copy the formula in Excel and change R or the frequency to compute the other required answers. Also, note that you must hand in the sheet of results and the sheet of formulas using the <ctrl-backquote/tilde> key (above the <tab> key).

Excel

2. Verify every hand calculation by simulating each circuit in PSpice using the given parameters. (See Appendix B for some tips on how to use PSpice efficiently.) Record the simulated results in the appropriate spaces. Specifically, you should add a column in your spreadsheet to record the simulated results. The hand calculations and simulated results should be the same (typically within 1%) and will be used when looking at the actual circuit measurements made in the lab. The schematic for every circuit needs to be printed out. If a parameter of a circuit is varied (for example, the value of a resistor changes), only print the circuit once for its initial parameters. In addition, print out the input/output waveforms for part 4 and part 5.2, as well as the circuit schematics for part 5.2. Attach these printouts to the lab. In the interest of saving paper, you may print more than one circuit schematic per page. (NOTE: **Your name must appear in the filename of all circuit and waveform printouts!**)

3. After both you and your lab partner have completed parts 1 and 2 above, compare answers, determine what the best answers are, and fill in the appropriate parts of the table for one copy of the In-Lab portion. (Only one copy needs to be handed in.) NOTE: All questions asked in this lab should be answered while actually doing the lab, after you have built the corresponding circuits and made measurements. In other words, you should **not** answer them before going to lab!

In-Lab Instructions (15pts)*Part One: RC Networks*

1. Assume $v_i(t) = \cos(\omega t)$ in the circuit in Figure 1, such that $f = \omega/(2\pi) = 10\text{kHz}$. Measure the phase shift in degrees between v_i and v_o for the following values of R in the RC network shown in Figure 1.

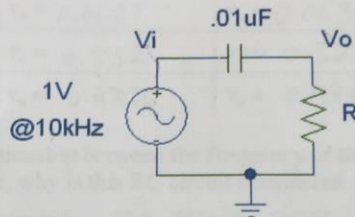


Figure 1: First RC Network

| Value of R (Ω) | Hand Calculation | PSpice Simulation | Circuit Measurement |
|-------------------------|-------------------|-------------------|-------------------------------|
| R = 1k | $\varphi = 57.86$ | $\varphi = 55.98$ | $\varphi = 57.6$ $\Delta 1.6$ |
| R = 2k | $\varphi = 38.52$ | $\varphi = 36.61$ | $\varphi = 39.6$ $\Delta 1$ |
| R = 5.6k | $\varphi = 15.87$ | $\varphi = 15.72$ | $\varphi = 14.4$ $\Delta 4$ |
| R = 10k | $\varphi = 9.04$ | $\varphi = 9.12$ | $\varphi = 10.8$ $\Delta 3$ |

To calculate phase shift on the oscilloscope, display both waveforms on the screen. Then press the "Cursor" button, set the "Type" to "Time," and adjust the two position knobs until one vertical cursor intersects the peak of the waveform of CH1 and the other cursor intersects the peak of the waveform of CH2. If you can't see the vertical cursor, adjust the knob until the cursor appears. The oscilloscope should show the time difference between these two peaks. Multiplying this time by the frequency (f , in Hz) of the signal and then again by 360 will give the phase shift in degrees.

Phase shift (degrees): $\varphi = t_{p-p} * f * 360$

Does v_o lead or lag v_i ? (Circle one.)

lead / lag

2. Using a $1k\Omega$ resistor for R , record the amplitude (1/2 the peak to peak) of the output voltage for the following three input voltage frequencies. (The amplitude of the input voltage should remain at 1V peak, i.e. 2V peak to peak)

| Frequency | Hand Calculation | PSpice Simulation | Circuit Measurement |
|-----------|------------------|-------------------|---------------------|
| 1kHz | $v_o = 0.0627$ | $v_o = 0.0631$ | $v_o = 0.072$ |
| 10kHz | $v_o = 0.532$ | $v_o = 0.52$ | $v_o = 0.526$ |
| 100kHz | $v_o = 0.9876$ | $v_o = 0.9912$ | $v_o = 0.98$ |

Based on the relationship between the frequency of the input voltage and the amplitude of the output voltage, why is this RC circuit considered a "high-pass" filter?

High Frequency can receive closer V_{out} , while lower frequency
cause low V_{out} to V_{in}
1V

3. In the circuit in Figure 2, again assume that $v_i(t) = \cos(\omega t)$, such that $f = \omega/(2\pi) = 10\text{kHz}$. Measure the phase shift between v_i and v_o for the following values of R in the RC network shown in Figure 2.

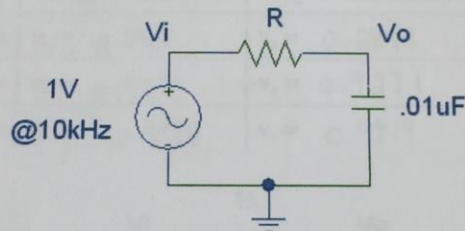


Figure 2: Second RC Network

| Value of R (Ω) | Hand Calculation | PSpice Simulation | Circuit Measurement |
|---------------------------|---------------------|--------------------|---------------------|
| $R = 1k$ | $\varphi = -32.142$ | $\varphi = -31.15$ | $\varphi = -32.4$ |
| $R = 2k$ | $\varphi = -51.488$ | $\varphi = -52.73$ | $\varphi = -50.4$ |
| $R = 5.6k$ | $\varphi = -74.135$ | $\varphi = -80.12$ | $\varphi = -75.6$ |
| $R = 10k$ | $\varphi = -80.957$ | $\varphi = -80.3$ | $\varphi = -79.2$ |

Does v_o lead or lag v_i ? (Circle one.)

lead / lag

4. Using a $1k\Omega$ resistor for R, record the output voltage for the following three input voltage frequencies. (The amplitude of the input voltage should remain at 1V peak.)

| Frequency | Hand Calculation | PSpice Simulation | Circuit Measurement |
|-----------|------------------|-------------------|------------------------------|
| 1kHz | $v_o = 0.99803$ | $v_o = 0.912$ | $v_o = 1.02$ |
| 10kHz | $v_o = 0.8467$ | $v_o = 0.736$ | $v_o = 0.92$ |
| 100kHz | $v_o = 0.1572$ | $v_o = 0.156$ | $v_o = \cancel{0.162} 0.162$ |

Based on the relationship between the frequency of the input voltage and the amplitude of the output voltage, why is this RC circuit considered a "low-pass" filter?

high frequency cause low V_{out} , lost V_{in} .

-1
what happens
to gain?

Part Two: RL Networks

1. Record the amplitude of the output voltage for the circuit shown in Figure 3, where $v_i(t) = \cos(\omega t)$, and f is the following three input voltage frequencies.

| Frequency | Hand Calculation | PSpice Simulation | Circuit Measurement |
|-----------|------------------|-------------------|---------------------|
| 1kHz | $v_o = 0.2832$ | $v_o = 0.2841$ | $v_o = 0.28$ |
| 10kHz | $v_o = 0.9472$ | $v_o = 0.9271$ | $v_o = 0.98$ |
| 100kHz | $v_o = 0.9995$ | $v_o = 0.9819$ | $v_o = 1.06$ |

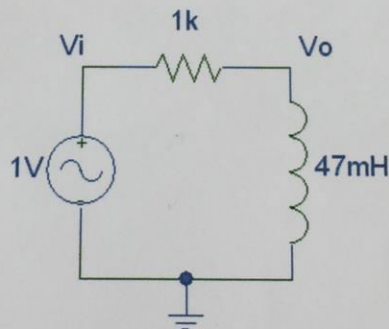


Figure 3: First RL Network

Based on the relationship between the frequency of the input voltage and the amplitude of the output voltage, would this circuit be considered a "low-pass" or a "high-pass" filter?

high pass / low pass

Does v_o lead or lag v_i ? (Circle one.)

lead / lag

2. Record the amplitude of the output voltage for the circuit shown in Figure 4, where $v_i(t) = \cos(\omega t)$, and f is the following three input voltage frequencies.

| Frequency | Hand Calculation | PSpice Simulation | Circuit Measurement |
|-----------|------------------|-------------------|---------------------|
| 1kHz | $v_o = 0.9591$ | $v_o = 0.961$ | $v_o = 0.910$ |
| 10kHz | $v_o = 0.3207$ | $v_o = 0.4101$ | $v_o = 0.335$ |
| 100kHz | $v_o = 0.0338$ | $v_o = 0.0312$ | $v_o = 0.06$ |

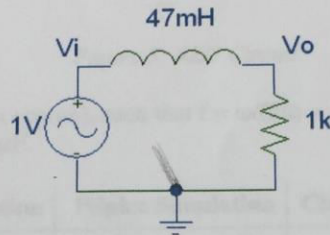


Figure 4: Second RL Network

Based on the relationship between the frequency of the input voltage and the amplitude of the output voltage, would this RL circuit be considered a “low-pass” or a “high-pass” filter?

high pass / low pass ✓

Does v_o lead or lag v_i ? (Circle one.)

lead / lag ✓

Part Three: Analysis of an RLC Circuit

1. Construct the RLC circuit shown in Figure 5.

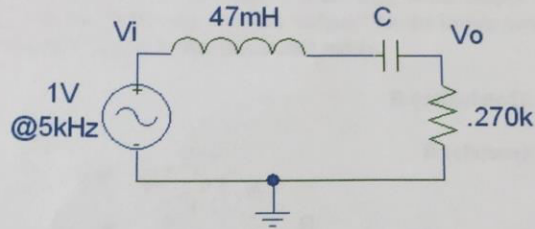


Figure 5: RLC Circuit

2. Assuming that $v_i(t) = \cos(\omega t)$, such that $f = \omega/(2\pi) = 5\text{kHz}$, measure the phase shift between v_i and v_o for $C = 0.01\mu\text{F}$.

| Hand Calculation | PSpice Simulation | Circuit Measurement |
|---------------------|-------------------|---------------------|
| $\varphi = 81.0095$ | $\varphi = 78.23$ | $\varphi = 79.2$ |

Does v_o lead or lag v_i ? (Circle one.)

lead / lag

3. Measure the phase shift between v_i and v_o for $C = 0.047\mu\text{F}$.

| Hand Calculation | PSpice Simulation | Circuit Measurement |
|-----------------------|-------------------|---------------------|
| $\varphi = -71.33511$ | $\varphi = -71.5$ | $\varphi = -72$ |

Does v_o lead or lag v_i ? (Circle one.)

lead / lag