
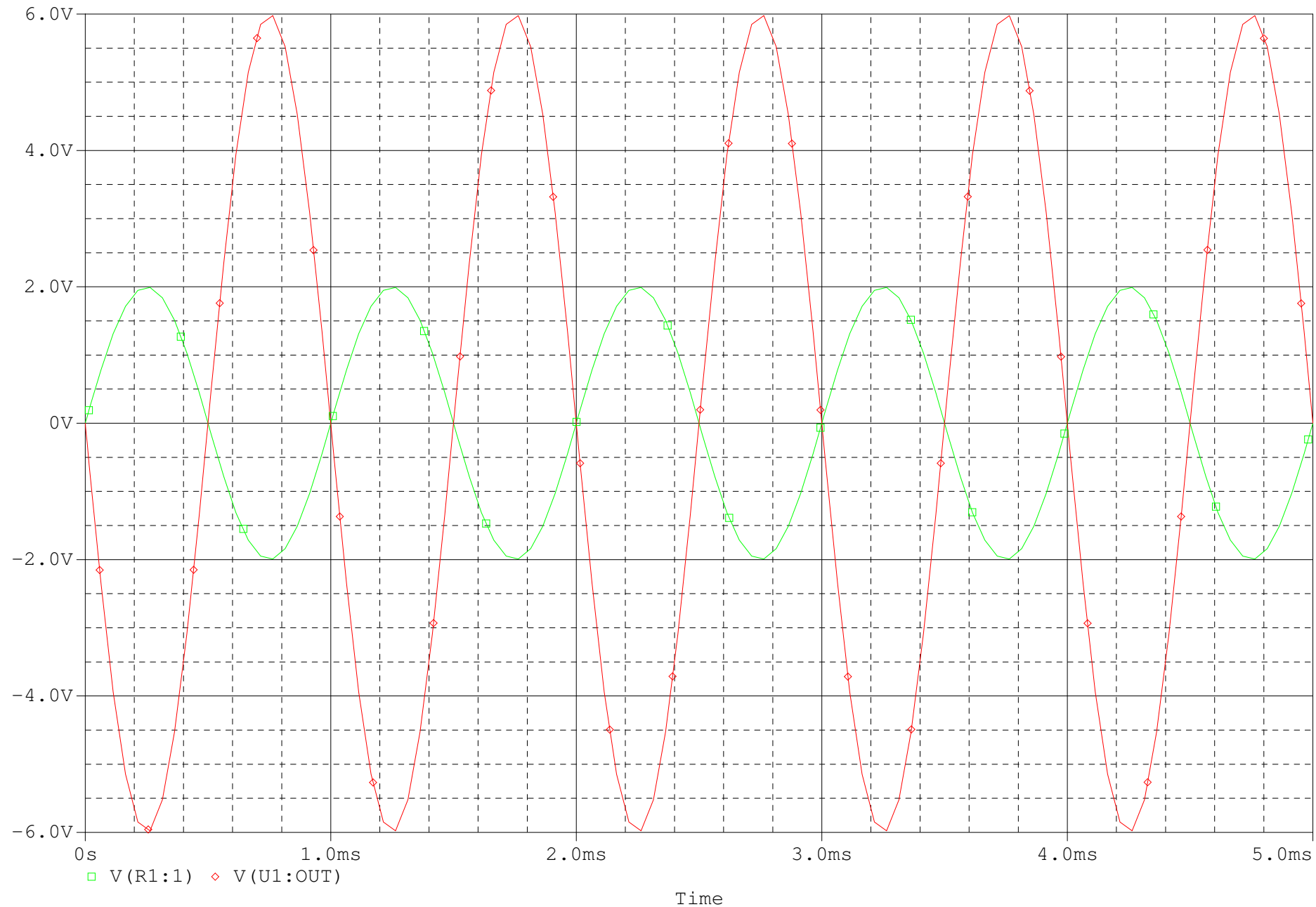


Title		
PreLab1 Xi Kun Zou		
Size	Document Number	Rev
A	<Doc>	<RevCo
Date:	Friday, February 10, 2017	Sheet 1 of 1

(A) 5.1.dat (active)

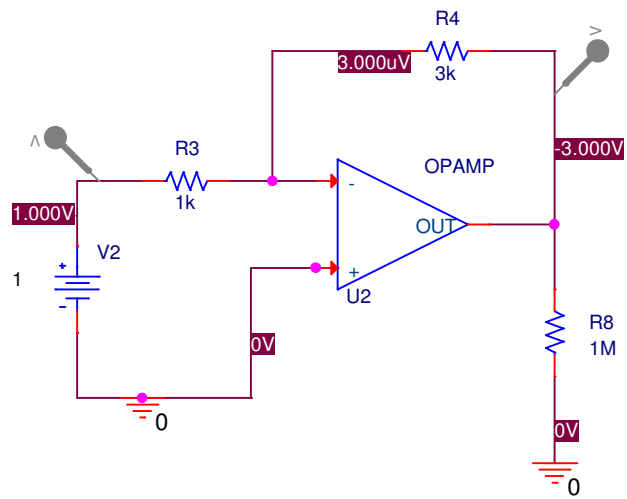



Title		
PreLab 5.2 Xi Kun Zou		
Size	Document Number	Rev
A	<Doc>	<RevCo>
Date:	Friday, February 10, 2017	Sheet 1 of 1

**** 02/10/17 05:45:56 ***** PSpice Lite (October 2012) ***** ID# 10813 ****

** Profile: "SCHEMATIC1-5.2sim" [C:\PExercice\Prelab52-PSpiceFiles\SCHEMATIC1\5.2sim.sim]

**** CIRCUIT DESCRIPTION

** Creating circuit file "5.2sim.cir"

** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT SIMULATIONS

*Libraries:

* Profile Libraries :

* Local Libraries :

* From [PSPICE NETLIST] section of C:\SPB_Data\cdssetup\OrCAD_PSpice\16.6.0/PSpice.ini file:

.lib "nomd.lib"

*Analysis directives:

.TRAN 0 1000ns 0

.OPTIONS ADVCONV

.PROBE64 V(alias(*)) I(alias(*)) W(alias(*)) D(alias(*)) NOISE(alias(*))

.INC "..\SCHEMATIC1.net"

**** INCLUDING SCHEMATIC1.net ****

* source PRELAB52

V_V2 N00968 0 1

E_U2 N00916 0 VALUE {LIMIT(V(0,N00950)*1E6,-15V,+15V)}

R_R4 N00950 N00916 3k TC=0,0

R_R3 N00968 N00950 1k TC=0,0

**** RESUMING 5.2sim.cir ****

.END

.

**** 02/10/17 05:45:56 ***** PSpice Lite (October 2012) ***** ID# 10813 ****

** Profile: "SCHEMATIC1-5.2sim" [C:\PExercice\Prelab52-PSpiceFiles\SCHEMATIC1\5.2sim.sim]

**** INITIAL TRANSIENT SOLUTION TEMPERATURE = 27.000 DEG C

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(N00916)	-3.0000	(N00950)	3.000E-06	(N00968)	1.0000		

VOLTAGE SOURCE NAME	CURRENTS CURRENT
---------------------	------------------

V_V2	-1.000E-03
------	------------

TOTAL POWER DISSIPATION	1.00E-03	WATTS
-------------------------	----------	-------

JOB CONCLUDED


.
**** 02/10/17 05:45:56 ***** PSpice Lite (October 2012) ***** ID# 10813 ****

** Profile: "SCHEMATIC1-5.2sim" [C:\PExcercise\Prelab52-PSpiceFiles\SCHEMATIC1\5.2sim.sim]

**** JOB STATISTICS SUMMARY

Total job time (using Solver 1) = .02

.

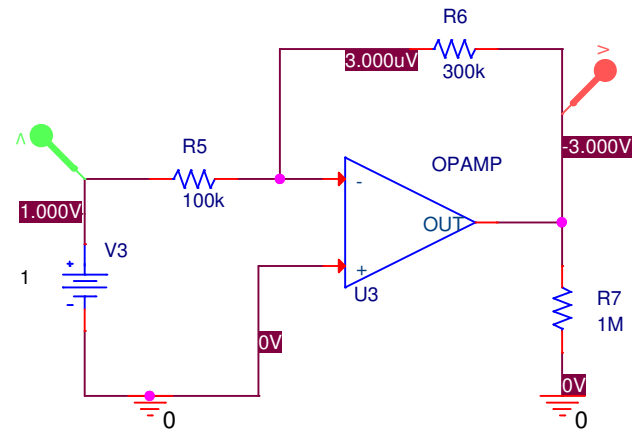

Title		
Xi Kun Zou 5.3		
Size A	Document Number <Doc>	Rev <RevCo>
Date: Friday, February 10, 2017	Sheet 1	of 1

```
.
**** 02/10/17 06:07:24 **** PSpice Lite (October 2012) **** ID# 10813 ****

** Profile: "SCHEMATIC1-5.3sim" [ C:\PExercice\plab53-PSpiceFiles\SCHEMATIC1\5.3sim.sim ]

****      CIRCUIT DESCRIPTION

*****

** Creating circuit file "5.3sim.cir"
** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT SIMULATIONS

*Libraries:
* Profile Libraries :
* Local Libraries :
* From [PSPICE NETLIST] section of C:\SPB_Data\cdssetup\OrCAD_PSpice\16.6.0/PSpice.ini file:
.lib "nomd.lib"

*Analysis directives:
.TRAN 0 1000ns 0
.OPTIONS ADVCONV
.PROBE64 V(alias(*)) I(alias(*)) W(alias(*)) D(alias(*)) NOISE(alias(*))
.INC "..\SCHEMATIC1.net"

**** INCLUDING SCHEMATIC1.net ****
* source PLAB53
V_V3      N01535 0 1
E_U3      N01495 0 VALUE {LIMIT(V(0,N01525)*1E6,-15V,+15V)}
R_R6      N01525 N01495 300k TC=0,0
R_R5      N01535 N01525 100k TC=0,0
R_R7      0 N01495 1M TC=0,0

**** RESUMING 5.3sim.cir ****
.END
.
**** 02/10/17 06:07:24 **** PSpice Lite (October 2012) **** ID# 10813 ****

** Profile: "SCHEMATIC1-5.3sim" [ C:\PExercice\plab53-PSpiceFiles\SCHEMATIC1\5.3sim.sim ]

****      INITIAL TRANSIENT SOLUTION      TEMPERATURE = 27.000 DEG C
```

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(N01495)	-3.0000	(N01525)	3.000E-06	(N01535)	1.0000		

VOLTAGE SOURCE NAME	CURRENTS CURRENT
V_V3	-1.000E-05

TOTAL POWER DISSIPATION	1.00E-05	WATTS
-------------------------	----------	-------


JOB CONCLUDED

•
**** 02/10/17 06:07:24 ***** PSpice Lite (October 2012) ***** ID# 10813 ****


** Profile: "SCHEMATIC1-5.3sim" [C:\PExcercise\plab53-PSpiceFiles\SCHEMATIC1\5.3sim.sim]

**** JOB STATISTICS SUMMARY

Total job time (using Solver 1) = .02

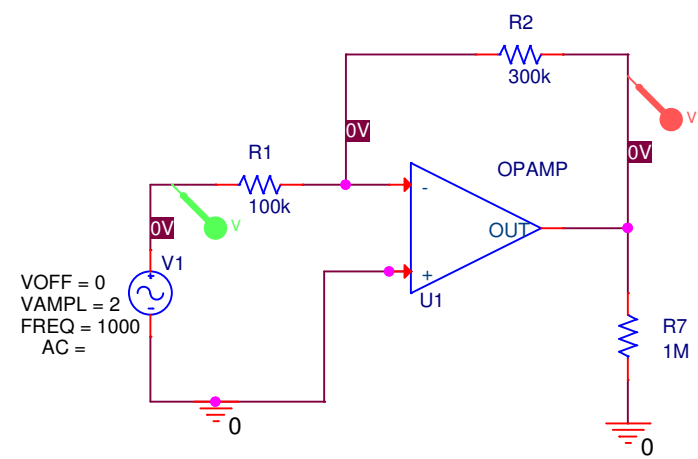

Title		
Xi Kun Zou 5.6		
Size	Document Number	Rev
A	<Doc>	<RevCo
Date:	Friday, February 10, 2017	Sheet 1 of 1

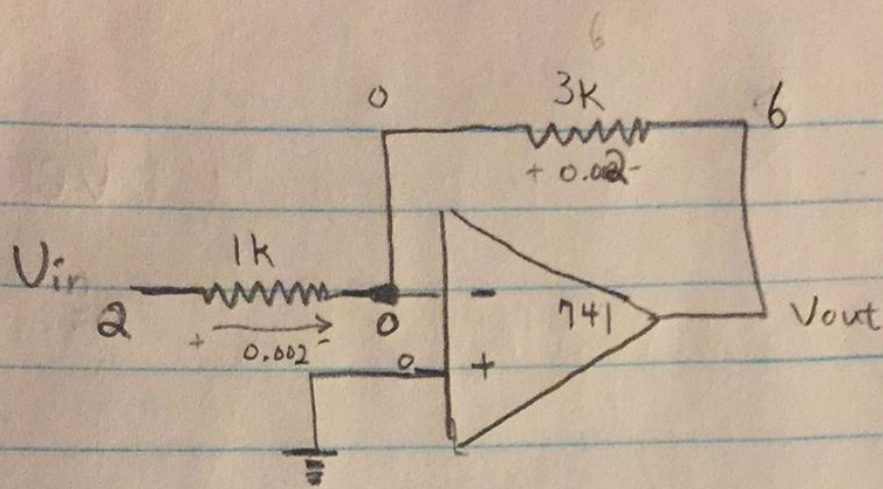

$$V_{in} = 2V$$

$$V_{out} = -6$$

$$\text{gain} = -6/2 = -3$$

For 100k & 300k case

$$i = \frac{2V}{100,000\Omega} = 0.00002A$$

$$V_{in} = 2V$$

$$V_{out} = 0.00002 \times 300,000 = 6V$$

$$\text{gain} = -\frac{6}{2} = -3$$

Part Five: Analysis of an Op-Amp Circuit

1. Consider the op-amp circuit in Figure 1. Compute the ratio V_{out}/V_{in} and record your values for V_{in} , V_{out} , and V_{out}/V_{in} in the spaces provided at the bottom of the page. The ratio V_{out}/V_{in} is called the *gain*. Next, simulate this circuit in PSpice with a 2V (peak-to-peak) 1kHz source for V_{in} and compute the gain. For this simulation, the ideal OPAMP will suffice. (You will need to place a large resistor, say 100k or 1M, connecting V_{out} to ground.) Record your values below.

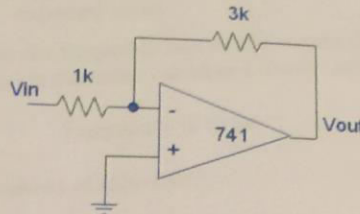


Figure 1: Op-Amp Circuit with a Fixed Gain

Construct the same circuit using a breadboard. The pin layout of the LM741 op-amp is shown in Figure 2. To wire the circuit as shown in the symbolic diagram of Figure 1, follow the wiring diagram shown in Figure 3. The 15V voltage source will come from the variable voltage source on the breadboard. The 1V (amplitude) sine wave will come from the function generator (the frequency can be set to 1kHz).

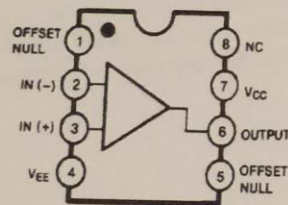


Figure 2:

Pin Layout of the LM741 Op-Amp

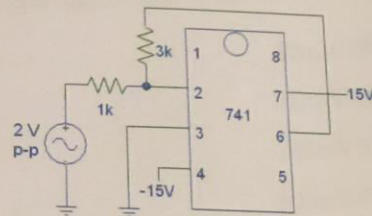


Figure 3:

Wiring Diagram for the Op-Amp Circuit

Build the circuit, but **before connecting the power, have a TA check the wiring of your circuit.**

Once the circuit is wired as shown in Figure 3, connect a probe from CH1 on the oscilloscope to the input voltage (coming from the function generator). Connect a second probe from CH2 on the oscilloscope to the output voltage (pin 6 of the op-amp). Display both readings on the oscilloscope. Record the peak-to-peak voltages below and compute the gain.

Quantity [units]	Hand Calculation	PSpice Simulation	Circuit Measurement
V_{in} [Vpp]	2V	2V	-1.96V
V_{out} [Vpp]	-6V	-6V	6V
gain (V_{out}/V_{in})	-3	-3	-3

1. (continued)

Looking at the positive and negative peaks of both signals, why is this op-amp considered to be "inverting"? What is the phase difference between V_{in} and V_{out} ?

When V_{in} is at minimum (-) V_{out} is at maximum (+)
by definition, the op-amp is inverting.
phase difference = 180°

2. Replace the 2V (pp) AC source with a 1V DC source. We do this to check the maximum power dissipated by the circuit. Run the simulation and this time check the output file (under the View menu). Near the bottom you should see the Total Power Dissipation. Record your value here.

Total Power Dissipation 0.001 W

3. Now, minimize power consumption while keeping the same gain across the amplifier, and also keeping V_{in} and V_{out} the same. Change only the two resistors, and be sure to only use resistors available in the lab for your simulation. (This is where the Electronics Lab Parts List is useful.) Design for a specification of 0.2mW. (In other words, make sure the power dissipated is less than this value.) Indicate the values you have chosen below.

R1 (which used to be 1k) 100k

R2 (which used to be 3k) 300k

4. Simulate the circuit in PSpice with the values chosen (and a 1V DC source), and verify that the gain has not changed and also that the design constraint has been met. Record the Total Power Dissipation from the output file here, and then fill out the appropriate spaces in part 6 on the next page.

Total Power Dissipation 0.01 mW

5. Before constructing the circuit, let's make sure you have the right resistors. Use the multimeter to measure each value of resistance and then compute the percent difference as compared to its labeled value. Comment on whether or not these resistors are within the labeled tolerances.

R1, tolerance _____

R1, measured _____

R1, % error _____

R2, tolerance _____

R2, measured _____

R2, % error _____

6. Construct the circuit with the values chosen, now using the 2V (pp) AC source, and verify that the gain is the desired value. Measure V_{in} and V_{out} , and compute the gain.

Quantity [units]	Hand Calculation	PSpice Simulation	Circuit Measurement
V_{in} [Vpp]	2V	2V	
V_{out} [Vpp]	-6V	-6V	
gain (V_{out}/V_{in})	-3	-3	

When you have completed the lab, sign and print your names below and have the TA initial next to each name.

TA

Appendix: Resistor Color Code Chart

Here is a chart to show you how to convert the colored bands on a resistor to a value of resistance and a tolerance.

4-Band-Code

2%, 5%, 10% 560k Ω \pm 5%

COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8		\pm 0.05%
White	9	9	9		
Gold				0.1 Ω	\pm 5% (J)
Silver				0.01 Ω	\pm 10% (K)

5-Band-Code

0.1%, 0.25%, 0.5%, 1% 237 Ω \pm 1%

(source: <http://www.digikey.com/~media/Images/Marketing/Resources/Calculators/resistor-color-chart>)